
Lab 8

Gerry Glynn

11/10/26


Down Counter

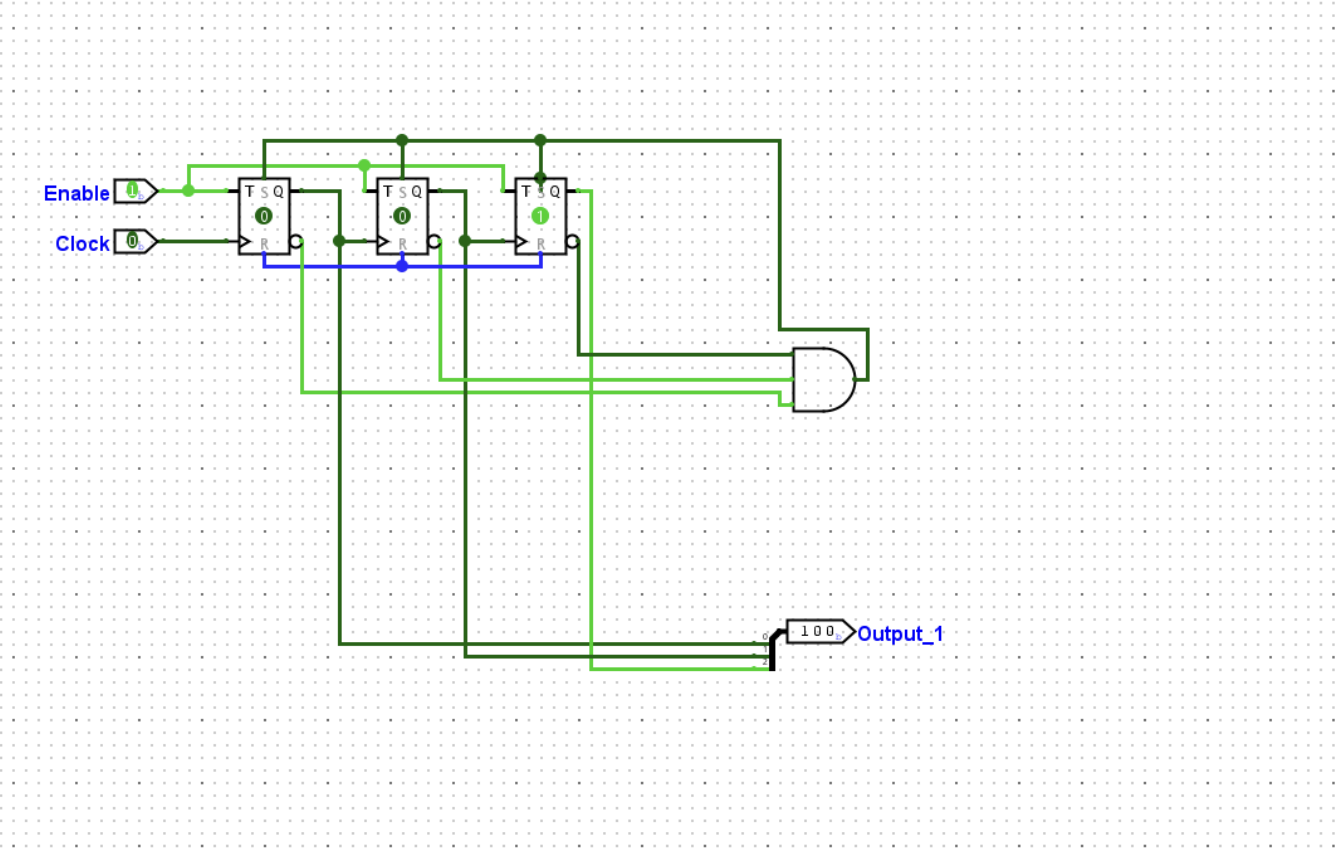- A Down Counter was made that cycles from 0-7 to be able to cycle 8 states.



FSM

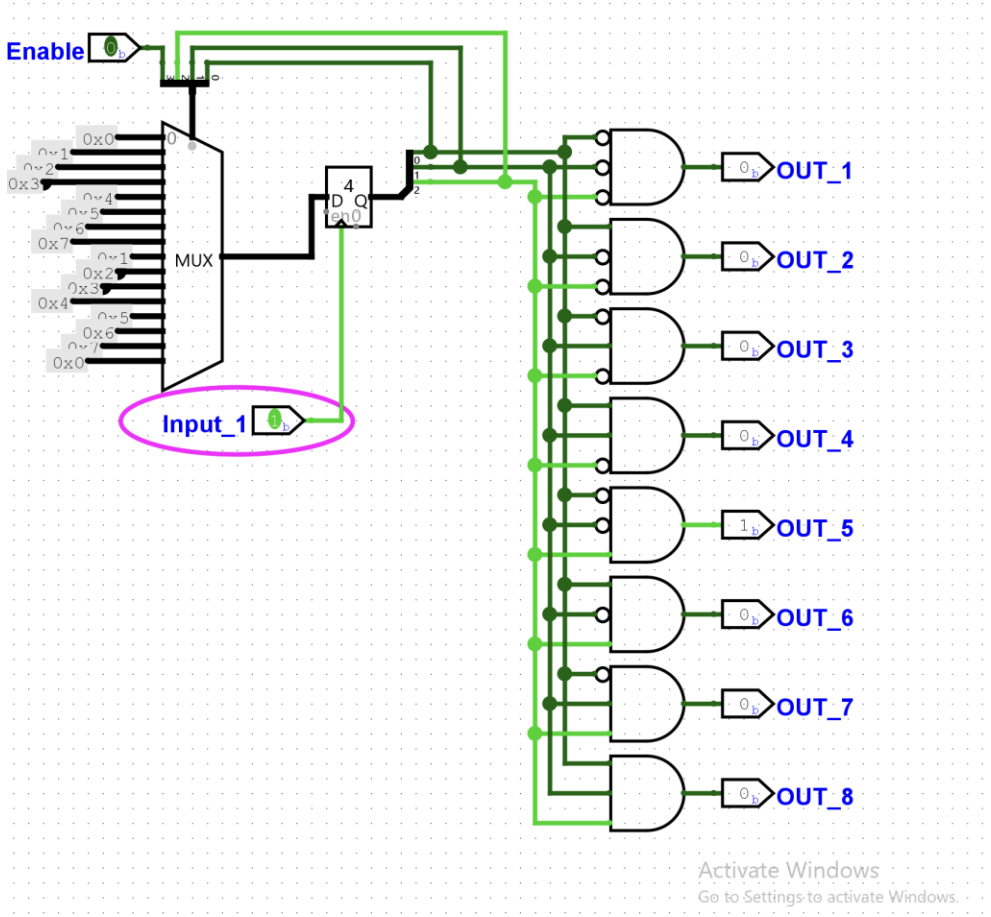The outputs will be connected to the LEDS. Some outputs will activate only 1 LED others will activate to one output will activate all 3.



Continuingg

- I will use a spliter to create clock variations.