
Final Project

Gerry Glynn

11/9/26

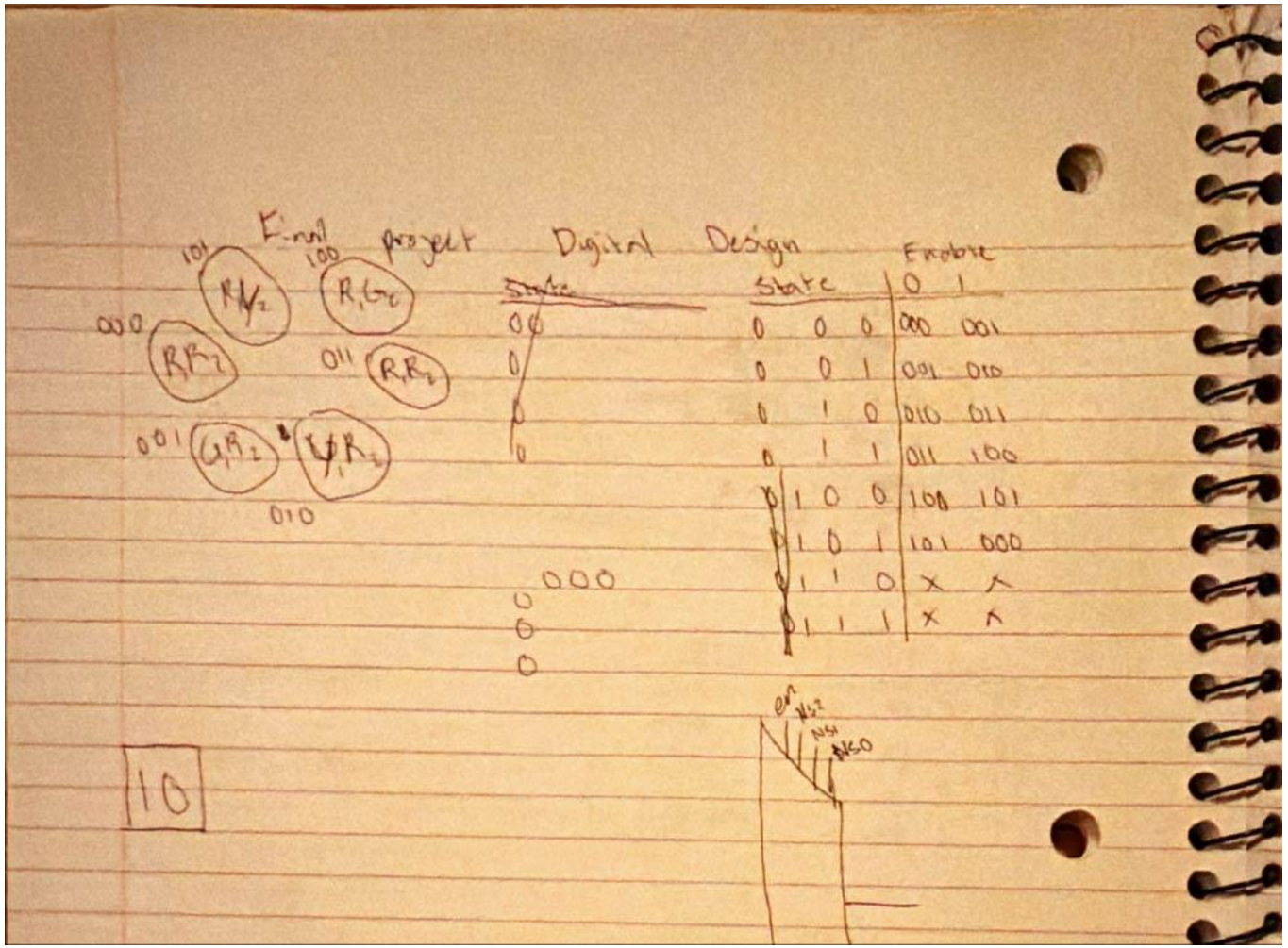



Paper drafting

- Drafting Ideas for the FSM

FSM

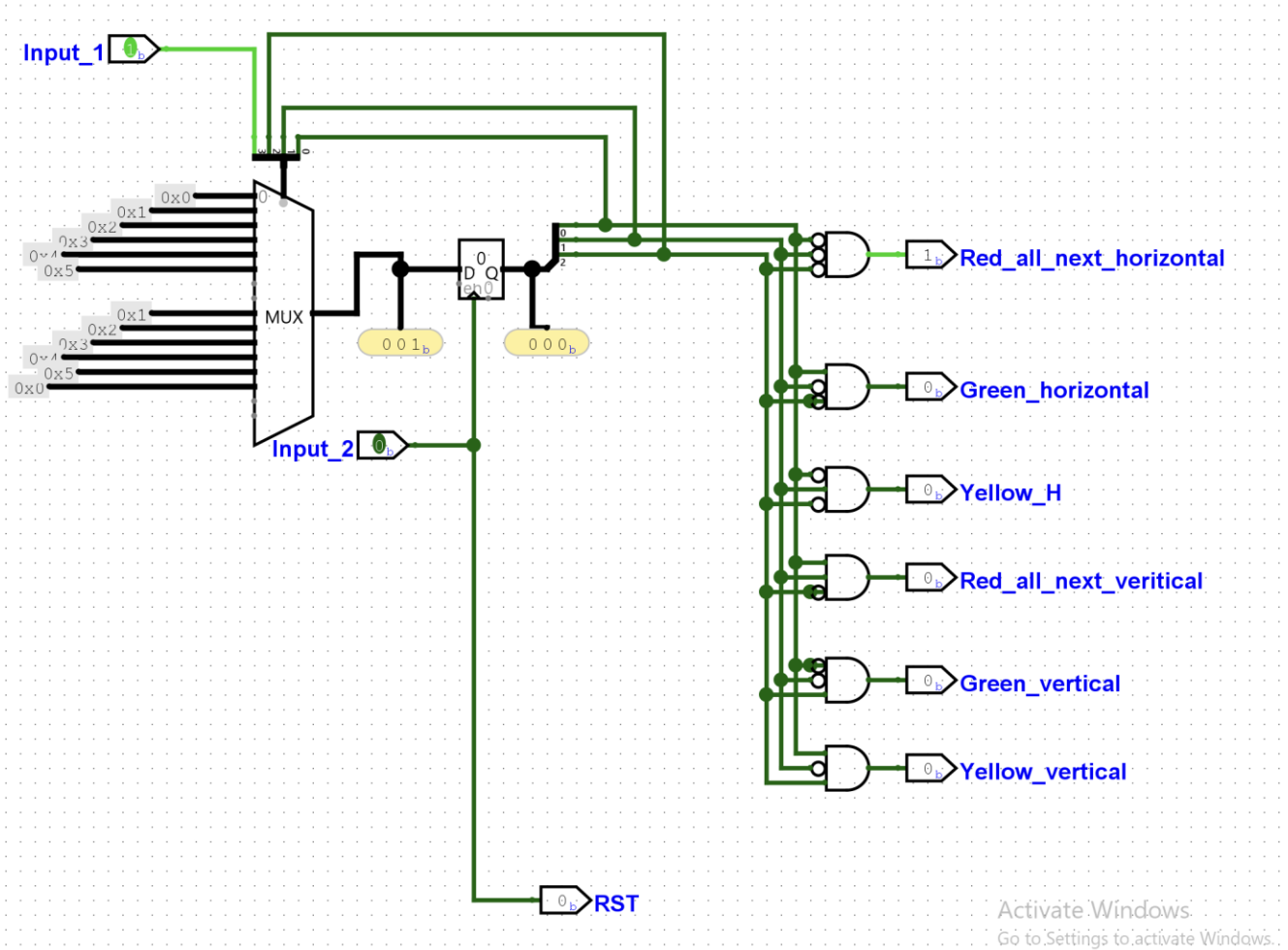I made the FSM with 6 states. For the 6 states that I wanted as the labels of the outputs.



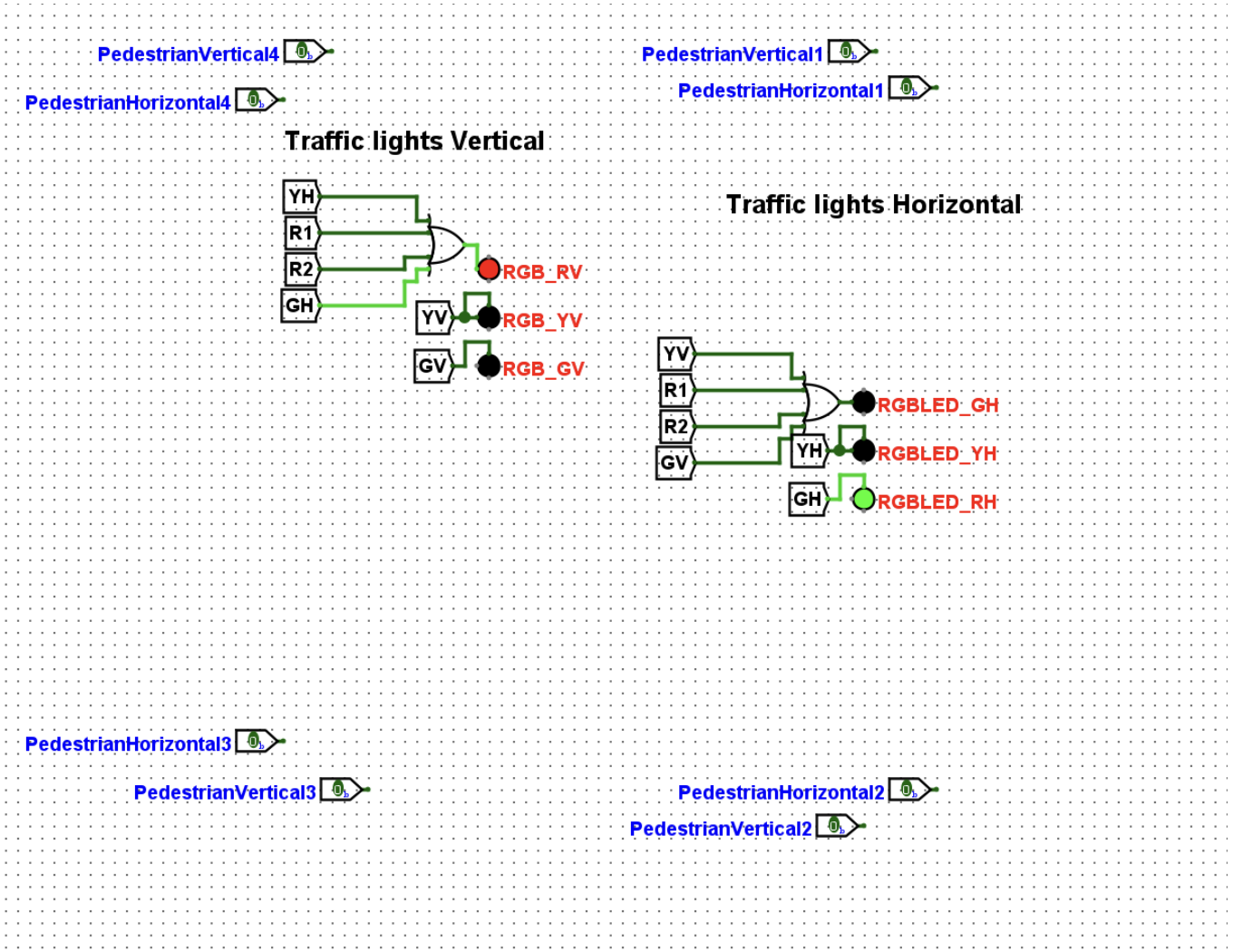

Connecting the lights

- I connected my FSM to the lights. Since I wanted one direction red at all times I added an or gate to the red LEDon both.

Walk timers

- They do not work. I need to figure out how to stop them at 0.

